

Homework policy: If I see something unusual about your work, you can be sure I will ask you about it. If you are unable to explain it to me why you chose some implementation method I will have to consider your entire solution wrong. Now, what is my definition of “unusual work”? Well, things like suspicious parts of code that may have been copied from a website or chunks of your implementation that are very close to one of your colleagues. I really encourage communication amongst yourselves, and I want you guys to have a good time learning while doing these exercises... but please don't blindly copy code. If you really must, at least acknowledge your sources.

1. Construct a circuit capable of comparing two 8-bit vectors, a and b . A selection pin (sel) should determine whether the comparison is signed ($sel = '1'$) or unsigned ($sel = '0'$). The circuit must have three outputs, $x1$, $x2$, and $x3$, corresponding to $a > b$, $a = b$, and $a < b$, respectively. See Figure 1 for a diagram of the proposed circuit.
2. **Extra-Credit:** Figure 2 shows the diagram of a very simple barrel shifter. In this case, the circuit must shift the input vector (of size 8) either 0 or 1 position to the left. When actually shifted ($shift = 1$), the LSB bit must be filled with '0' (shown in the bottom left corner of the diagram). If $shift = 0$, then $outp = inp$; else, if $shift = 1$, then $outp(0) = '0'$ and $outp(i) = inp(i + 1)$, for $1 \leq i \leq 7$. Write a concurrent code for this circuit.

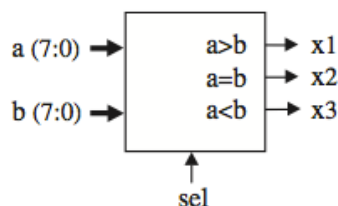


Figure 1

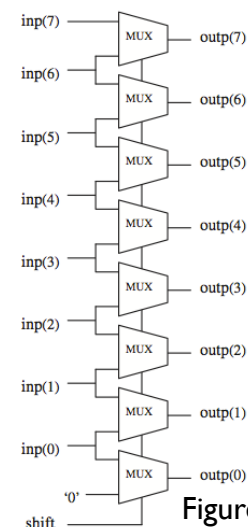


Figure 2